
 


Decoders


remember:

 

2x4 Decoder Cascade




d0	d1	ena	0	1	2	3
X	X	0	0	0	0	0
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	1

 


Each output maps to a State (one-hot encoding)

↳ states will cycle through

3x8 Decoder Cascade

 


d0	d1	d2	ena	0	1	2	3	4	5	6	7
X	X	X	0	0	0	0	0	0	0	0	0
0	0	0	1	1	0	0	0	0	0	0	0
0	0	1	1	0	1	0	0	0	0	0	0
0	1	0	1	0	0	1	0	0	0	0	0
0	1	1	1	0	0	0	1	0	0	0	0
1	0	0	1	0	0	0	0	1	0	0	0
1	0	1	1	0	0	0	0	0	1	0	0
1	1	0	1	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	0	1

 


You can use AND gates to do the same logic - use the same logic table

 
(We wanted to try this instead since it's more explicit to describe in verilog)



each AND gate controls 1 bit

 

All and gates have 3 inputs and enable

 


→ Verilog: out[7] = ena & inb[7] & inb[2] & inb[3]

Adder


(1 bit full adder)

A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Summer

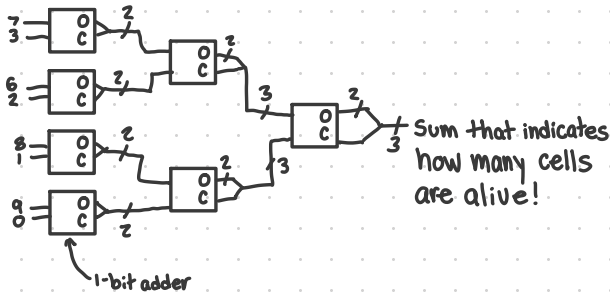
input 8-bit bus from main
↳ split into 4 2 input adders



Conway's Game of Life Cell Module

Rules:

 
- 1) Any cell w/ 2-3 neighbors survive
- 2) Any dead cell w/ 3 neighbors is born
- 3) All other live cells die in the next generation, dead cells stay dead



represented by 8-bit bus supplied by main

Neighbour Count	Sum out			alive current	alive next
	0	1	2		
0	0	0	0	0	0
1	0	0	1	0	0
2	0	1	0	0	0
3	0	1	1	0	1
4-7	1	X	X	0	0
0	0	0	0	1	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	1	1
4-7	1	X	X	1	0

& logic

 

LED DRIVER

note:

rows need to go low to light up the LED

